KCSE CLUSTER TESTS 11

Physics Paper 3

1.

You are provided with the following apparatus:

Converging lens

- ✓ A suitable lens holder.
- ✓ A candle.
- ✓ A mounted white screen
- ✓ A metre rule

Procedure as follows:

a) Arrange the apparatus as shown in the figure 1(a) below such that the candle flame and the centre of the lens lie in a straight line. Set the distance u =22.5 cm



Figure 1(a)

b) Adjust the position of the screen until a sharp image of the object is just observed on it.

c) Measure and record the distance V in Table 1.

υ	22.5	25.0	32.5	35.0	40.0	45.0
V cm						

d) Repeat the experiment for the other values of v and record your results in the table.

- e) On the grid, plot a graph of V (y-axis) against v. Draw the best fit curve. (5marks)
- f) Draw a line to bisect the origin (0, 0) to meet the curve at a point c. (1mark)
- g) Given that the focal length –f- of the lens used = $\frac{0x+0y}{4}$ find the value of f correct your answer to 2 significant figures. (2s.f) (3marks)

h) Set up the apparatus as shown in figure below.



20 marks

2.

You are provided with the following apparatus:-

• 100cm nichrome wire mounted on a metre rule labelled MN.

Compiled & distributed by Schools Net Kenya, P.O. Box 15509-00503, Nairobi | Tel:+254202319748 E-mail: infosnkenya@gmail.com | ORDER ANSWERS ONLINE at <u>www.schoolsnetkenya.com</u>

- An ammeter.
- A voltmeter.
- Three dry cells.
- Cell holder.
- A switch.
- Eight connecting wires(at least 4 with crocodile clips at the end)
- A torch bulb fixed into a lamp holder.

Procedure

a) Connect the apparatus provided as shown in the circuit below.



b) Place the sliding contact at C, 25 cm from M, and then close the switch. Take the ammeter and the voltmeter readings.

Length L	I(A)	Pd(V)	I(mA)	Pd(mV)	Log I	Log V
(cm)						
5						
25						
40						
60						
70						
90						
	•	•	•	•	•	(8t

c) Repeat the above experiment by placing the sliding contact C at 5 cm, 40 cm, 60cm, 70 cm and 90 cm. Record your readings and complete the table below.

d) Find logarithms of mA and mV i.e milliAmperes and milli volts respectively.

e) i) Plot a graph of log I(y –axis) against log V.

ii) Determine the slope of the graph.

f) Given the relation

I=K^{∨n}

Using your graph determine the values of K and n.



20 marks